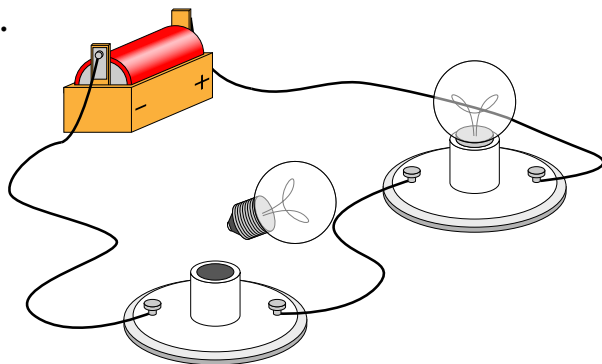


Name: _____


Electrical Circuits

Tell whether the light bulb or bulbs will light or will not light based on the circuit.


1.




2.

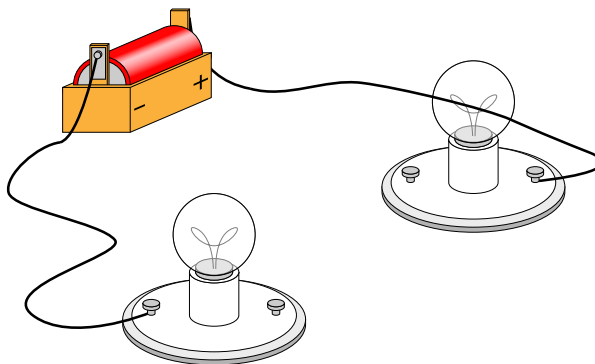


3.

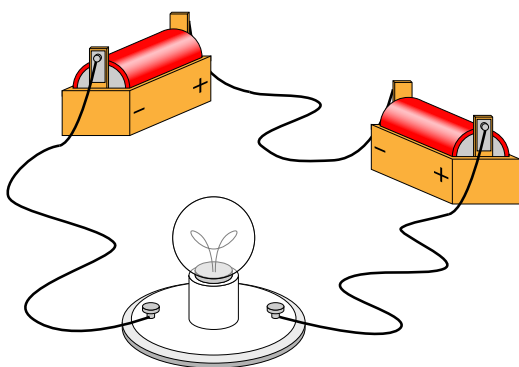


4.

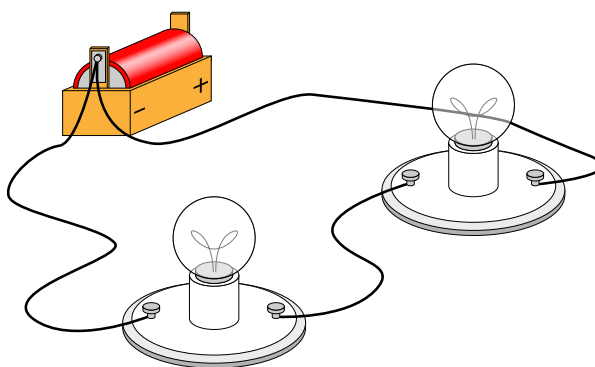

5.

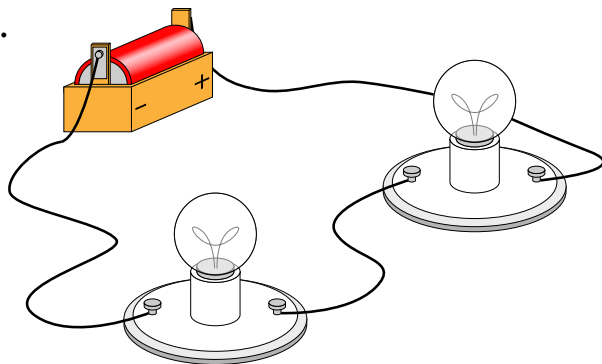

6.

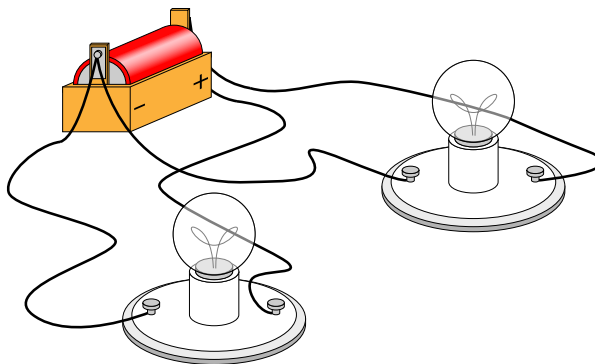


ANSWER KEY

Electrical Circuits


Tell whether the light bulb or bulbs will light or will not light based on the circuit.

1.

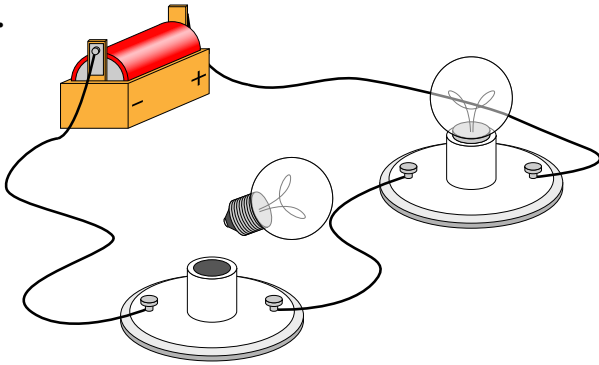


will not light

2.

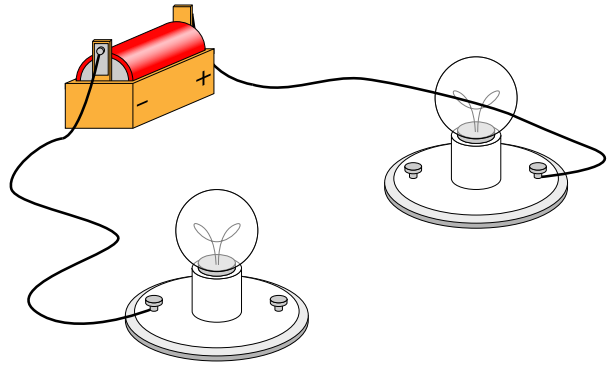


will not light

3.

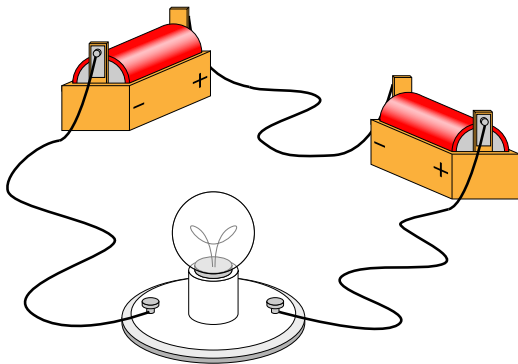


will light

4.

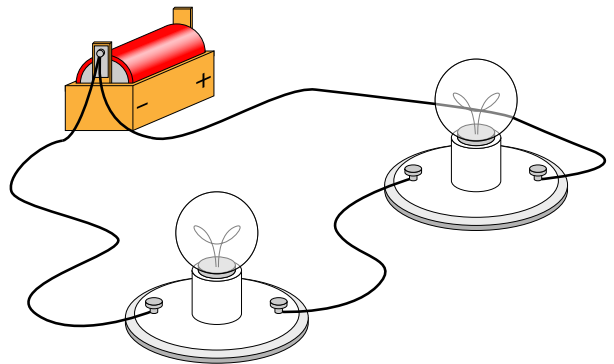


will not light

5.

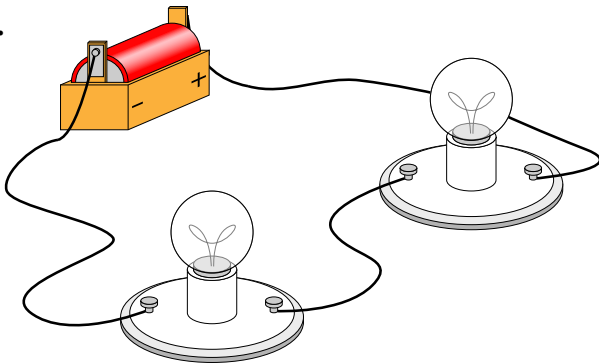

will light

6.

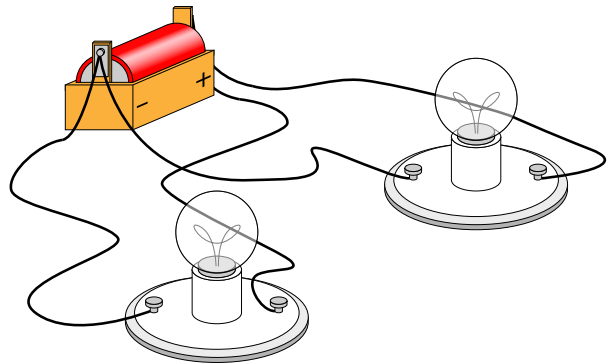

will light